

## Difference Amplifier

Friday, September 14, 2007  
11:32 AM

1) Observation:

$$A_{v \text{ non inverting Amp}} = 1 + \frac{R_2}{R_1}$$

$$2) A_{v \text{ inverting Amp}} = - \frac{R_2}{R_1}$$


Combine (1) + (2) to design an  
Difference Amplifier

But we must make the two  
gain magnitude equal so  
common mode signals are  
rejected. Idea

Attenuate to gain of the  
positive path from  $\left\{ 1 + \frac{R_2}{R_1} \rightarrow \frac{R_2}{R_1} \right\}$


Based on Fig (1)



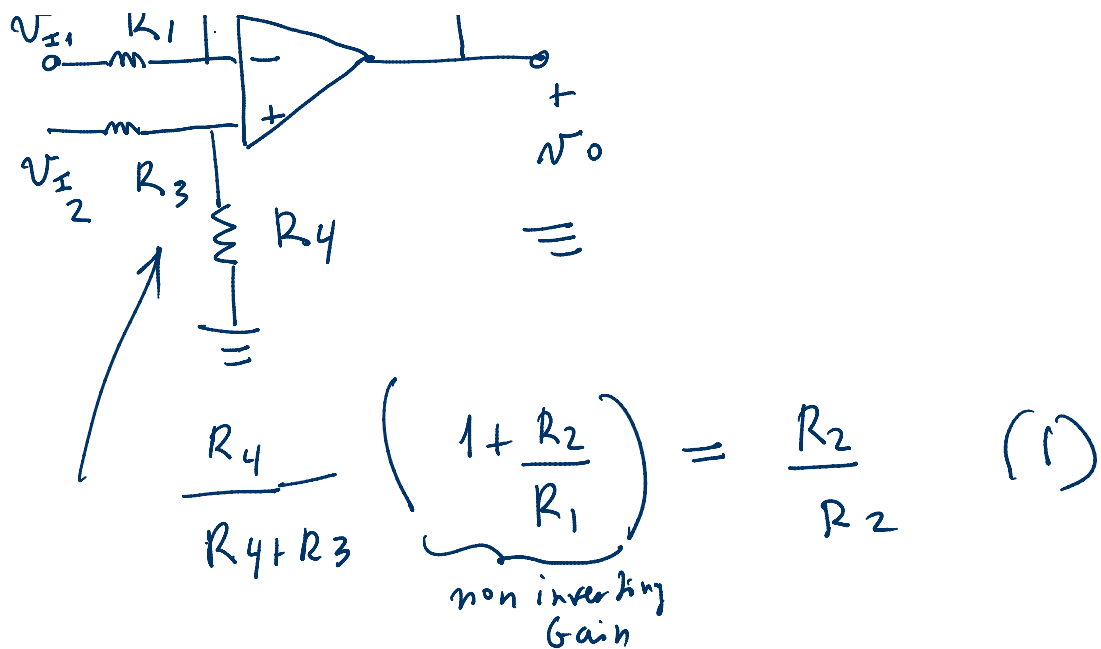


Apply superposition principle:  
i.e. add solutions separately  
(a)

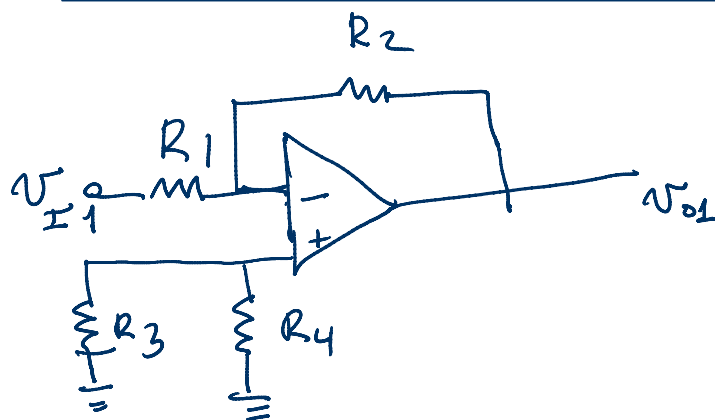ground  $v_{i2} \Rightarrow$  inverting configuration solution



$$v_{o1} = - \frac{R_2}{R_1} v_{i1} \quad (2)$$

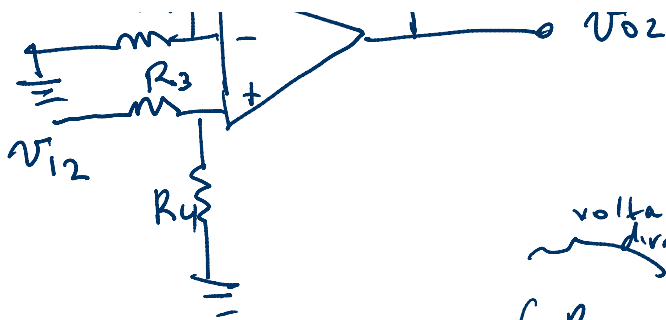(b) Ground  $v_{i1} \Rightarrow$  non inverting configuration solution



$$V_o = V_{i2} \left( \frac{R_4}{R_4 + R_3} \right) \left( 1 + \frac{R_2}{R_1} \right) \quad (3)$$

voltage divider      non-inverting gain

but

$$= \left( \frac{R_2}{R_1} \right) V_{i2} \quad (4)$$

(in order to make equal the two gain amplitudes).

Eq(1) can be put in the form :

$$\frac{R_4}{R_4 + R_3} = \frac{R_2}{R_2 + R_1}$$

where  
 $R_4 = R_2$   
 $R_3 = R_1$

Based on superposition principle.

$$\begin{aligned} V_o &= \frac{R_2}{R_1} (V_{i2} - V_{i1}) \\ &= \frac{R_2}{R_1} (V_{Id}) \end{aligned}$$