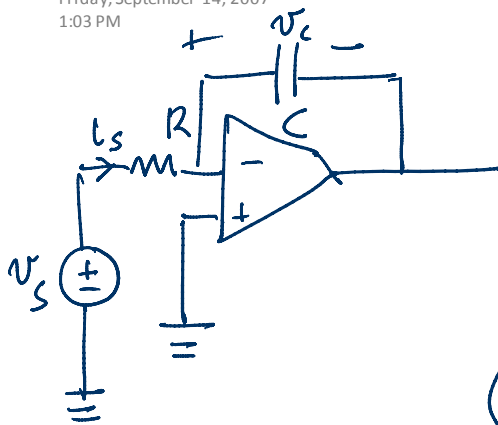


Integrator-Differentiator

Friday, September 14, 2007
1:03 PM



inverting amp
with a capacitor
replacing feedback
resistor, R_F

$$L_S = \frac{v_s}{R} \quad (1)$$

$$L_C = -C \frac{dv_o}{dt} \quad (2)$$

For an ideal amp:

$$L = 0 \Rightarrow L_C = L_S \quad (3)$$

Equating (1) & (2)

& integrating

$$\int dv_o = \int -\frac{1}{RC} dv_s d\tau$$

integral
of input
voltage


$$\text{or } v_o = -\frac{1}{RC} \int v_s(\tau) d\tau + v_o(0)$$

initial
capacitor
voltage

in which $v_o(0)$ is determined

by the voltage of the capacitor at
 $t = 0$: $v_o(0) = V_C(0)$

DIFFERENTIATOR

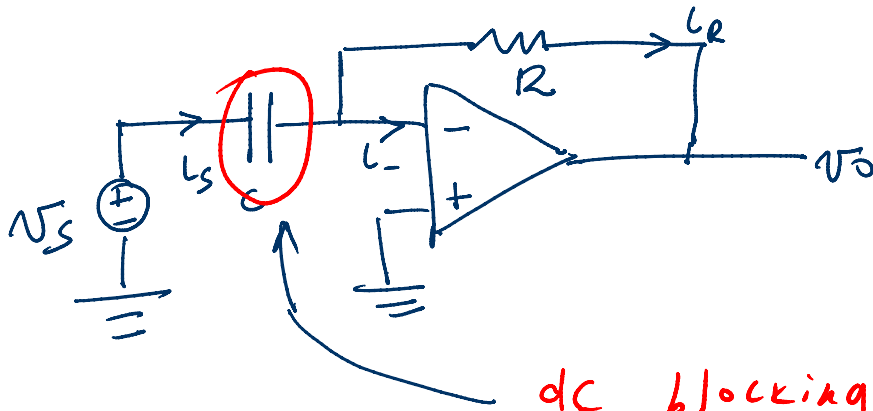

$$L_s = C \frac{dv_s}{dt}$$

$$L_R = - \frac{v_o}{R}$$

dc blocking
capacitor \Rightarrow
high frequency
components of the
signal are emphasized

$$\text{Since } L_- = 0 \Rightarrow I_s = I_R$$

$$\Rightarrow v_o = -RC \frac{dv_s}{dt}$$

\Rightarrow Output voltage scaled
derivative of the input voltage.