


## Difference Amplifier:

- ① Amplifies the difference between two signals
- ② Rejects common signals to the input (i.e. noise/interrference signals)

let  $v_{Id} = v_2 - v_1 = \text{differential input signal}$  (1)

$$v_{Icm} = \frac{1}{2} (v_1 + v_2) = \text{average of common-mode input signal}$$
 (2)

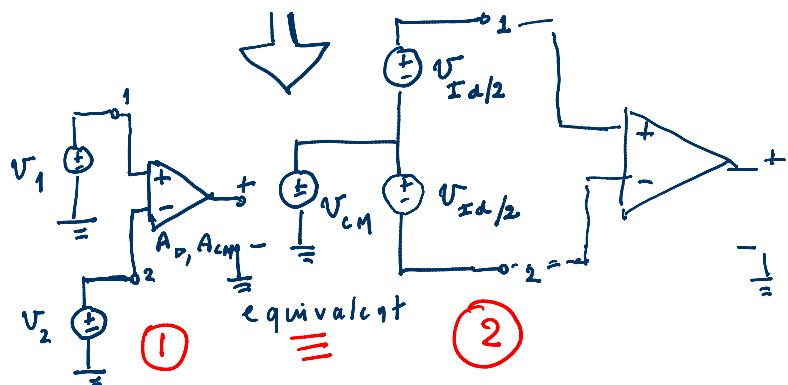let  $\left\{ \begin{array}{l} v_1 = v_{Icm} - v_{Id}/2 \\ v_2 = v_{Icm} + v_{Id}/2 \end{array} \right.$



$$v_o = A_d v_{Id} + A_{cm} v_{Icm} = A_d (v_{Id} + \frac{A_{cm}}{A_d} v_{Icm}) = A_d (v_{Id} + \frac{v_{Icm}}{CMRR})$$


where  $A_d = \text{amplifier differential gain}$

$A_{cm} = \text{common-mode gain}$

where

$$\text{CMRR} = 20 \log \frac{|A_d|}{|A_{cm}|} \text{ dB}$$

example

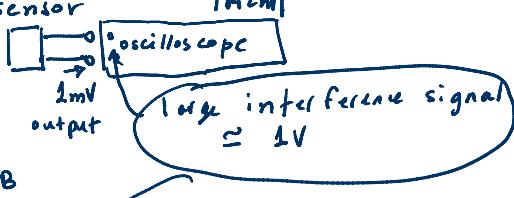

$$60 \leq \text{CMRR} \leq 120 \text{ dB}$$

dB

utilize a difference amplifier to remove the interference signal.

### Examples

Referring to Fig (1)

let  $A_d = 2500$

$CMRR = 80 \text{ dB}$

$V_1 = 5.001 \text{ V}$

$V_2 = 4.99 \text{ V}$

Find  $V_o$ ?

$CMRR \rightarrow$  convert to number

$$CMRR = 10^{\frac{80 \text{ dB}}{20}} = \pm 10^4$$

Let  $CMRR = 10^4$

$$V_{Id} = 5.001 \text{ V} - 4.99 \text{ V} = 0.002 \text{ V}$$

$$V_{ICM} = \frac{5.001 + 4.99}{2}$$

$$V_o = A_d \left[ V_{Id} + \frac{V_{ICM}}{CMRR} \right] = 2500 \left[ 0.002 + \frac{5.001}{10^4} \right] \text{ V}$$


$$= 2500 [0.002 + 0.0005 \text{ V}] = 6.25 \text{ V}$$

Inverting Amplifier - Input/Output Resistance

① Calculate  $R_{IN}$

②

Calculate  $R_{out}$

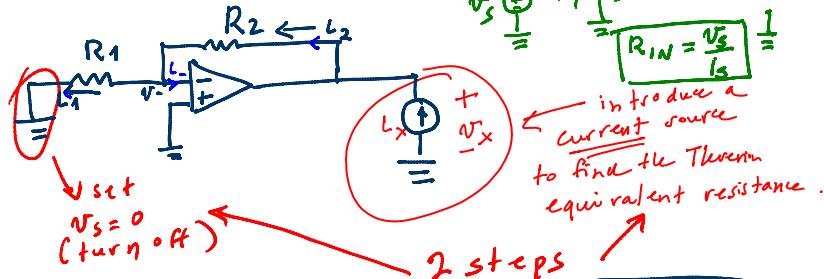

$$R_{out} = \frac{V_x}{I_x}$$

Assumption 1  
 $V_{IL} = 0$   
Assumption 2  
 $I_{+} = 0$   
 $I_{-} = 0$

$$V_x = L_2 R_2 + I R_1$$

$$L_+ = L_1 + L_2$$

$$\text{but } L_+ = 0 \Rightarrow L_1 = L_2 \\ \Rightarrow V_x = L_1 (R_2 + R_1)$$

$$\left\{ L_1 = \frac{V_x}{R_1} \right\} \text{ but } L_1 = 0 \text{ since } V_- = 0 \text{ (assumption 1)}$$

$$\Rightarrow V_x = 0 \Rightarrow R_{out} = 0$$

## Design of an Inverting Amplifier

Choose  $R_1, R_2$  so that to have  
an input resistance of  $20 \text{ k}\Omega$   
and a gain of  $40 \text{ dB}$

recall

$$R_{IN} = R_1$$

$$A_v = -\frac{R_2}{R_1}$$

Steps:  $R_{IN} = R_1 = 20 \text{ k}\Omega \quad \checkmark$

Convert  $\text{dB}$  to a number

$$|A_v| = 10^{\frac{40\text{dB}}{20\text{dB}}} = 100$$


$$\Rightarrow A_v = -100$$

now,  $R_1 = R_{IN} = 20 \text{ k}$

$$A_v = -\frac{R_2}{R_1} \Rightarrow R_2 = 100 R_1$$

$$= 2 \text{ M}\Omega$$

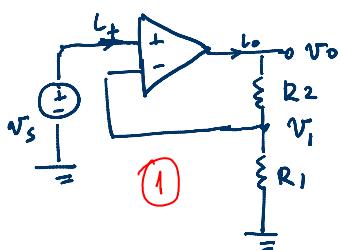
Non-Inverting Amplifier input/output  
Resistance



$$R_{IN} = \frac{V_s}{I_+} = \infty \quad (I_+ = 0)$$


$$R_{OUT} = 0 \quad (\text{apply again a test current source to the output})$$

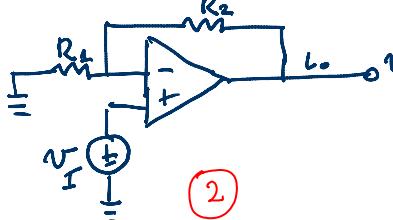Recall the above diagram is  
equivalent to :



$$\text{Gain} = A_v = 1 + \frac{R_2}{R_1}$$

Unity-Gain Buffer

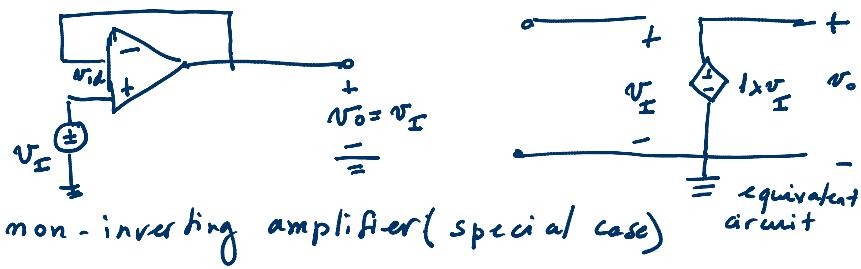

$$R_2 = \frac{V_+}{V_I} = \infty$$

$$R_2 = 0$$

$$\text{Now } A_V = 1 + \frac{R_2}{R_1} = 1$$

Alternative derivation:

$$V_I - V_{I,d} = V_O$$

but  $V_{I,d} = 0$  (first criterion)

$$\Rightarrow V_I = V_O$$

### Design of a non-Inverting Amplifier

Find:  $A_V$

$$V_D$$

of the amplifier (2) given:

$$R_1 = 3 \text{ k}\Omega$$

$$R_2 = 43 \text{ k}\Omega$$

$$V_S = +0.1V$$

$$A_V = 1 + \frac{R_2}{R_1} = 1 + \frac{43 \text{ k}\Omega}{3 \text{ k}\Omega} = +15.3$$

$$V_O = A_V V_S = (15.3)(0.1V) = 1.53V$$


$$I_o = \frac{V_o}{R_2 + R_1} = \frac{1.53V}{43 \text{ k} + 3 \text{ k}} = 33.3 \mu\text{A}$$

Summary of the ideal inverting & non-inverting Amplifiers

Inverting Amp      Noninverting Amp.

Voltage gain	$- \frac{R_2}{R_1}$	$1 + \frac{R_2}{R_1}$
Input resistance	$R_1$	$\infty$
Output resistance	0	0
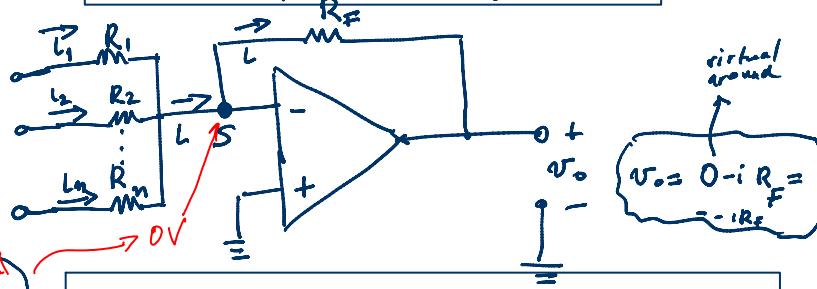
### The Summing Amplifier (Weighted Summer)



$$V_O = - \left( \frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \dots + \frac{R_F}{R_n} v_n \right)$$


it means that although voltage = 0 still there is a current flow.

How did we find this formula?  
[SUPERPOSITION PRINCIPLE].

Simply we have an array of inverting amplifiers, which produce currents  $i_1, i_2, \dots, i_n$  that are added at which are forced to flow through  $R_F$ .

What about if we sum signals that have opposite polarity?

We must use two inverting amplifiers.

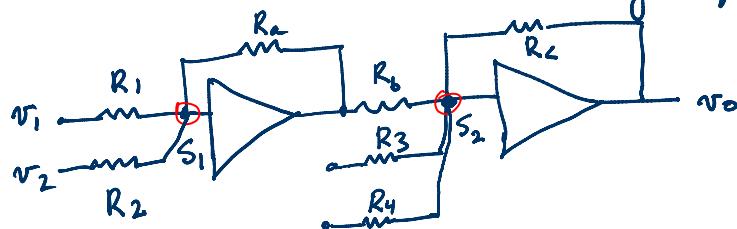

$$V_O = V_1 \left( \frac{R_a}{R_1} \right) \left( \frac{R_c}{R_b} \right) + V_2 \left( \frac{R_a}{R_2} \right) \left( \frac{R_c}{R_b} \right) - V_3 \left( \frac{R_c}{R_3} \right) - V_4 \left( \frac{R_c}{R_4} \right)$$