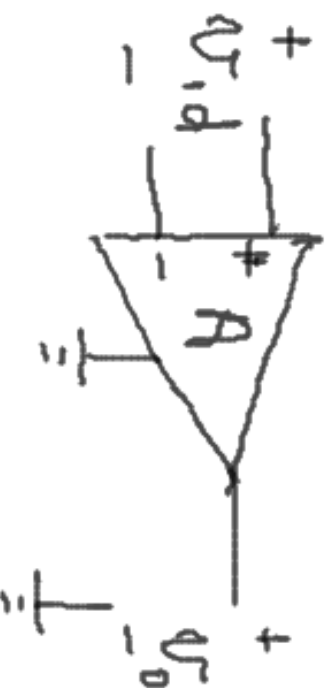


DIFFERENTIAL AMPLIFIER


It responds to the difference of two input signals



$$v_o = A v_{i,d}$$

Differential Amplifiers

General Consideration

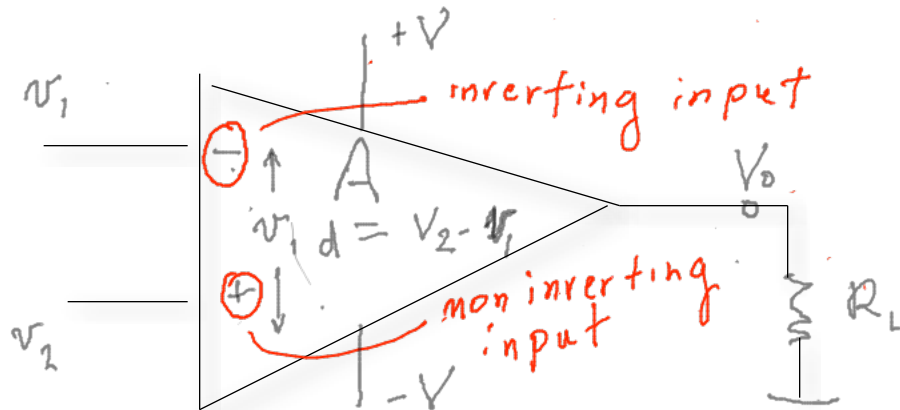

It amplifies the difference of two input signals

$$v_d = v_2 - v_1 = \text{voltage to be amplified}$$

v_1 = the voltage applied to the inverting input

v_2 = the voltage applied to the non inverting input


The output of the Amp depends from:

1. Gain of the Amp
2. The polarity relationship between v_1 & v_2
3. The values of the supply voltage $+V, -V$
4. The load resistance, R_L

A = voltage gain, open-circuit voltage gain.

This is the gain without feedback path from the output to the op input

DIFFERENTIAL AMPLIFIER MODEL

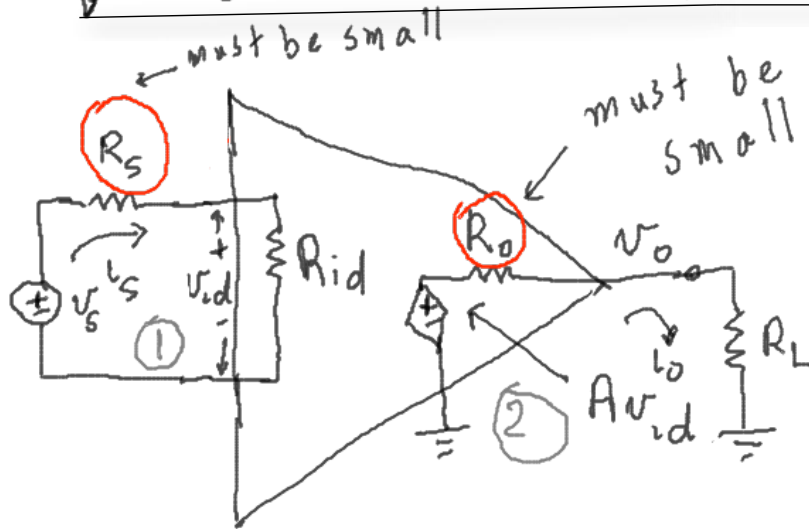

R_s = source resistance

v_s = Thevenin equivalent voltage

A = voltage gain

v_{id} = differential input signal voltage

R_{id} = amplifier input resistance

R_o = amplifier output resistance.

We must prove that:

$$A_v = \frac{v_o}{v_s} = A \frac{R_{id}}{R_s + R_{id}} \frac{R_L}{R_o + R_L}$$

an ideal amplifier should be independent of R_s, R_L so that

$$R_s \ll R_{id}$$

$$R_o \ll R_L$$

We look at circuits ① & ②

Goal: find $A_v = \frac{v_o}{v_s}$

Steps: find v_s, v_o

①

$$v_{id} = i_s R_s \quad (1)$$

Eliminate i_s

$$v_s = v_{R_s} + v_{id}$$

$$= i_s (R_s + R_{id})$$

$$i_s = \frac{v_s}{R_s + R_{id}}$$

□

Since $v_{id} = i_s R_{id} \quad (1)$

\Rightarrow

$$v_{id} = \frac{v_s}{(R_s + R_{id})} R_{id} \quad (2)$$

From circuit ②

$$v_o = i_o R_L \quad (3)$$

Eliminate i_o

$$A v_{id} = v_{R_o} + v_o$$

$$= i_o (R_o + R_L) \Rightarrow i_o = \frac{A v_{id}}{R_o + R_L} \quad (4)$$

Therefore:

$$V_o = \frac{A v_{id}}{(R_o + R_L)} R_L \quad (5)$$

Combining (2) & (5)

$$\begin{aligned} A_v = \frac{V_o}{v_s} &= \frac{A \cancel{v_{id}} R_L}{(R_o + R_L)} \frac{R_{id}}{\cancel{v_{id}} (R_s + R_{id})} \\ &= A \underbrace{\frac{R_{id}}{(R_s + R_{id})}}_{\text{input circuit parameters}} \underbrace{\frac{R_L}{(R_o + R_L)}}_{\text{output circuit parameters}} \quad (6) \end{aligned}$$

IDEAL DIFFERENTIAL AMPLIFIERS

$$\left. \begin{array}{l} R_{id} = \infty \\ R_{out} = 0 \end{array} \right\} \text{conditions (7)}$$

looking at (6)

$$\left. \begin{array}{l} A_v = A \\ v_o = A v_{id} \end{array} \right\} \quad (8)$$

{ since

Realistically speaking, max v_o can be achieved when

$$\left. \begin{array}{l} R_{id} \gg R_s \\ R_o \ll R_L \end{array} \right\} \text{fully mismatched resistance condition} \quad (9)$$

Conditions of an Ideal Op Amp

special case of the ideal difference Amp.

$$\left. \begin{array}{l} R_{id} = \infty \\ R_o = 0 \\ \text{voltage gain, } A = \infty \end{array} \right\} \quad 10$$

$$v_{id} = \frac{v_o}{A} \quad \& \quad \lim_{A \rightarrow \infty} v_{id} = 0 \quad (11)$$

$$\text{if } A = \infty \Rightarrow v_{id} = 0 \quad (12)$$

ASSUMPTION 1

$$\text{if } R_{id} = \infty \Rightarrow i_+ , i_- = 0 \quad (13)$$


ASSUMPTION 2

These two assumptions form the basis of the ideal OP Amp.

Additional Assumptions

Infinite common-mode rejection
Infinite output voltage range
Infinite open-loop bandwidth
Infinite slew-rate
Zero output resistance

INVERTING AMPLIFIER

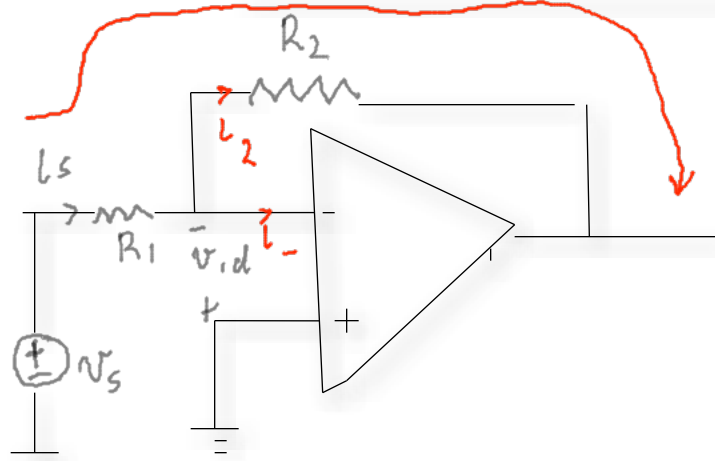

- Ground the positive input of the Amp.
- introduce a feedback network consisting of 2 resistors R_1, R_2

Goal

find $A_v = \frac{V_o}{V_s}$

$$V_s = L_s R_1 + L_2 R_2 + V_o \quad (1)$$

Now

$$L_s = L_1 + L_2$$

$$= L_2 \quad \text{since } L_1 \approx 0$$

(2)
according to assumption 2

\Rightarrow

$$V_s = L_s (R_1 + R_2) + V_o \quad (3)$$

$$L_s = \frac{V_s - V_-}{R_1} \quad (4)$$

V_- : voltage at the inverting input

but $V_{id} = V_+ - V_- = 0$

Since $V_+ = 0$

$\Rightarrow V_- = 0$

therefore $L_s = \frac{V_s}{R_1} \quad (5)$

$5 \rightarrow 3$

$$V_s = V_s + \frac{V_s R_2}{R_1} + V_o \Rightarrow \frac{V_s R_2}{R_1} + V_o = 0$$

or $V_o = -V_s \frac{R_2}{R_1}$

\Rightarrow $A_v = \text{voltage gain}$ (6)
 $= -\frac{R_2}{R_1}$

▪ Negative gain indicates 180° phase shift between input & output signal

A_v depends from the choice of

R_1 & R_2

if $R_2 > R_1$ $A_v > 1$

$R_1 > R_2$ $A_v < 1$

The input resistance (from Eq 5)


$R_{IN} = \frac{V_s}{I_s} = R_1$ (7)

output
resistance

$R_o = 0$ (8)

NON INVERTING AMPLIFIER

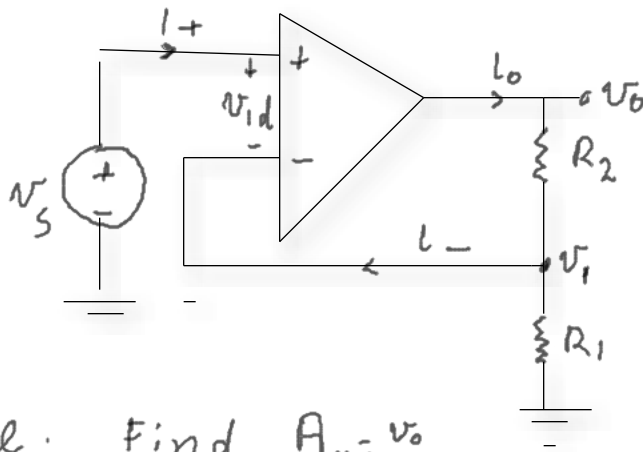The input signal is applied to the noninverting input.
Portion of the output signal is fed back to the negative input terminal



Goal: Find $A_v = \frac{v_o}{v_s}$

$$\left. \begin{array}{l} i_- = 0 \\ i_+ = 0 \end{array} \right\} \text{Assumption 2}$$

$$v_i = v_o \frac{R_1}{R_1 + R_2} \quad (1)$$

$$v_s = v_d + v_i \quad (2)$$

$$\text{but } v_d = 0 \quad (\text{assumption 1})$$

$$\Rightarrow v_s = v_i \quad (3)$$

$$3 \rightarrow 1$$
$$v_s = v_o \frac{R_1}{R_1 + R_2} \quad A_v \gg 1$$

$$\Rightarrow A_v = \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \quad (4)$$

